

# Intro to Measurement Systems

LA-CoNGA physics

February 3, 2021



## **PRACTICE 1: PMT signal conditioning circuit**

Dennis Cazar Ramírez  
email: [dcazar@usfq.edu.ec](mailto:dcazar@usfq.edu.ec)

# Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Objectives</b>	<b>2</b>
<b>3</b>	<b>Activities</b>	<b>2</b>
3.1	Signal amplifier . . . . .	2
3.2	Peak detector . . . . .	3
3.3	Simulations . . . . .	3
<b>4</b>	<b>Report</b>	<b>3</b>
<b>5</b>	<b>References</b>	<b>4</b>

# 1 Introduction

A photomultiplier (PMT) is the most popular transducer in High Energy Particle (HEP) detection application. A PMT produce an electric pulse proportional to the intensity of light produced by the interaction of a HEP particle with matter (water for a Water Cerenkov detector for example). The basic task in detecting HEP particle is to calculate the rate, i.e. count the amount of particles arriving at the detector in a certain time. Rate is measured in Hertz and depends of several factors, see ref(1).

In this activity you have to design and simulate a peak detector circuit which be used to convert the PMT signal to an impulse suitable for a digital system which will perform the counting task.

Some of the contents needed to this work you already know, others must be studied during this activity

# 2 Objectives

- Main Objective: Design and simulate a PMT signal conditioning circuit
- Activities:
  - To design a signal amplifier with op amps
  - Learn about a peak detection techniques
  - To design an amplifier and peak detection circuit
  - To simulate the circuit and show results

# 3 Activities

## 3.1 Signal amplifier

PMT signal is a negative pulse of few tenths of milivolts height and microseconds wide, an example is shown in the following figure:

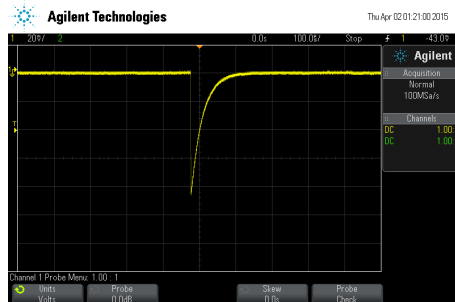


Figure 1: Actual signal from a 9” PMT working at 1200V HV nominal level

This "original" signal must be inverted and amplified to a hundred of millivolts range to be compatible with an analog to digital converter ADC or any digital circuit used to record and post process this signal. Take into account that a typical PMT signal voltage range could be from 20mV to 200mV

A replica of this signal must be created and stored in a voltage source (function generator) in LTSpice, see ref(2).

Design a circuit that inverts and amplifies the signal, choose the right op-amp model, factors as *slew rate* could be important, see ref (3)

### 3.2 Peak detector

A signal diode is the key component of a peak detector, a simple rectifier circuit could act as a peak detector but it has limitations.

For this activity you have to explore active peak detector circuits based on a combination of diodes and op amps, see ref(4).

The parameters of this circuit depend on the output characteristics of the signal amplifier designed earlier.

### 3.3 Simulations

Simulate the whole circuit and test it for different levels of signals, try to change the pulse width and height of the PMT signal to determine:

- What is the narrowest signal your circuit can detect
- What is the input range of your peak detector

## 4 Report

Write a detailed report of these activities focusing on how you can use these circuits to build a cosmic ray particle detector, see ref(5)

## 5 References

1. [Cosmic Ray Detectors: Principles of Operation and a Brief Overview of \(Mostly\) U.S. Flight Instruments](#)
2. [LTspice: Piecewise Linear Functions for Voltage & Current Sources](#)
3. [Understanding Operational Amplifier Slew Rate](#)
4. [Op Amp Rectifiers, Peak Detectors and Clamps](#)
5. The desktop Muon Detector: A simple, physics-motivated machine- and electronics-shop project for university students, S.N. Axani, J.M. Conrad and C. Kirby, 2017