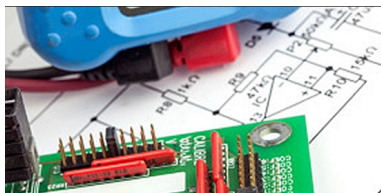


# LA-CoNGA physics Introduction to Measurements Systems Basic Concepts

by Dennis Cazar Ramírez

January 26, 2023

# Contents



- Basics [Electric Vocabulary](#)
- Voltage and current
- Kirchoff's Laws
- Circuit elements
- Exercises

# Current & Voltage

- We start our study of electronics with definitions and the basic laws that apply to all circuits
- In electronics, we are interested in keeping track of two basic quantities: the currents and voltages in a circuit.
- If you can make these quantities behave like you want, you have succeeded.
- **Current** measures the flow of charge past a point in the circuit. The units of current are thus coulombs per second or amperes, abbreviated as  $A$ . In this text we will use the symbol  $I$  or  $i$  for current.
- The work per unit charge required to move some charge between two points is called the **voltage** between those points. The units of voltage are thus joules per coulomb or volts, abbreviated  $V$ . In this text we will use the symbol  $V$  or  $v$  for voltage.

# Kirchoff's Laws

- The sum of the currents into a node (i.e. any point on the circuit) equals the sum of the currents flowing out of the node. This is **Kirchoff's Current Law (KCL)** and expresses conservation of charge.

$$\sum_k^n I_k = 0 \quad (1)$$


where the sum is over all currents into or out of the node.

- The sum of the voltages around any closed circuit is zero. This is **Kirchoff's Voltage Law (KVL)** and expresses conservation of energy. In equation form,

$$\sum_k^n V_k = 0 \quad (2)$$
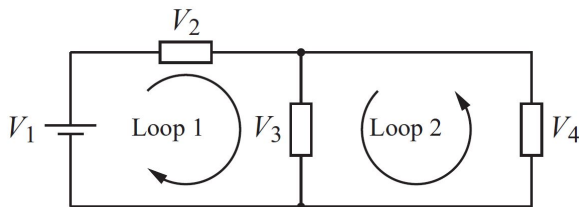
# Kirchoff's Laws

- We must use a convention to define the signs of the currents and voltages



- The power  $P$  provided or consumed by a circuit device is given by

$$P = IV \quad (3)$$


The units of power are thus joules per second or watts, abbreviated  $W$

# Resistors

## I-V characteristic

- A common way to represent the behavior of a circuit device is the  $I$ - $V$  characteristic. This is a plot of the current  $I$  through the device as a function of applied voltage  $V$  across the device.
- The resistor has a simple linear  $I$ - $V$  characteristic (Ohm's Law)

$$V = IR \quad (4)$$

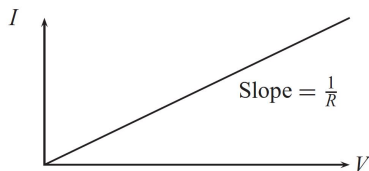

The constant of proportionality,  $R$ , is called the resistance of the device

# Resistance

- The resistance of the device depends only on its physical properties – its size and composition. More specifically:

$$R = \rho \frac{L}{A} \quad (5)$$

where  $\rho$  is the resistivity,  $L$  is the length, and  $A$  is the cross-sectional area of the material.

Material	$\rho(10^{-8}\Omega m)$
Silver	1.6
Copper	1.7
Nichrome	100
Carbon	3500

**Table:** The resistivity of some common electronic materials

# Types of Resistors

- Resistors can be of a fixed or variable value



Resistor



Rheostat



Potentiometer

Schematic symbols for a fixed resistor and two types of variable resistors.



Shaft Potentiometer



Precision Shaft Potentiometer



Trim Potentiometer



Slide Potentiometer



Linear Potentiometer



Hollow Shaft Potentiometer



# Equivalent circuit laws for resistors

## Series and parallel

- When forming equivalent circuits, any number of resistors in series may be replaced by a single equivalent resistor given by:

$$R_{eq} = \sum_i^n R_i \quad (6)$$

The current  $I$  in any series element is the same.


- When forming equivalent circuits, any number of resistors in parallel may be replaced by a single equivalent resistor given by:

$$\frac{1}{R_{eq}} = \sum_i^n \frac{1}{R_i} \quad (7)$$

All elements connected in parallel are at the same voltage  $V$ .

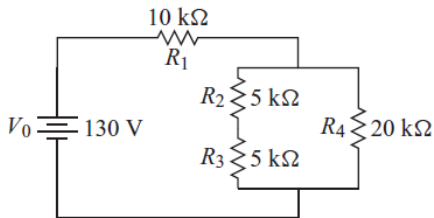
# Finding an equivalent circuit

- For the circuit shown, how much current flows through the  $20\text{K}$  resistor? What must its power rating be?


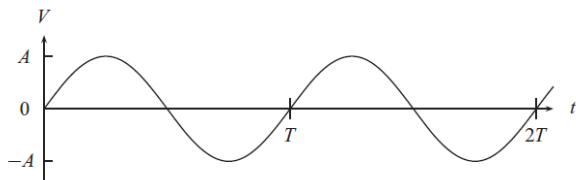
# AC signals

- So far our examples have used constant voltage sources such as batteries. Constant voltages and currents are described as *DC* quantities in electronics.
- On the other hand, voltages and currents that vary in time are called *AC* quantities. For future reference, we list here some of the most common *AC* signals.
- Sinusoidal signals. This is probably the most fundamental signal in electronics since, as we will see later, any signal can be constructed from sinusoidal signals



$$V = A\sin(2\pi ft + \phi) = A\sin(\omega t + \phi) \quad (8)$$

# AC signals

## Sinusoidal signals

There are several ways to specify the amplitude of a sinusoidal signal that are in common use. These include the following:

- The peak amplitude  $A$  or  $A_p$ .
- The peak-to-peak amplitude  $A_{pp} = 2A$ .
- The rms amplitude  $A_{rms} = A/\sqrt{2}$ . This is useful for power calculations involving sinusoidal waves.

$$P = \frac{1}{T} \int_0^T \frac{V^2}{R} dt = \frac{1}{TR} \int_0^T A^2 \sin^2(\omega t + \phi) dt = \frac{A_{rms}^2}{R} \quad (9)$$


- Decibels (abbreviated dB) are used to compare the amplitude of two signals, say  $A_1$  and  $A_2$ :

$$dB = 20 \log_{10} \frac{A_2}{A_1} = 10 \log_{10} \left( \frac{A_2}{A_1} \right)^2 = 10 \log_{10} \frac{P_2}{P_1} \quad (10)$$


# AC signals
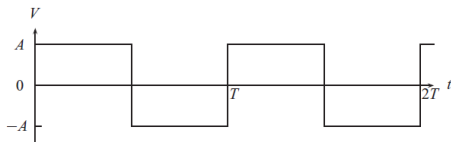
## Other signals

- Square wave. Specified by an amplitude and a frequency (or period).



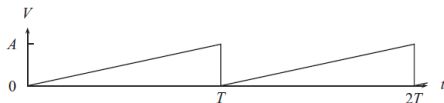
- Sawtooth wave. Specified by an amplitude and a frequency (or period).




# AC signals
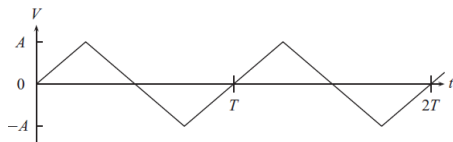
## Other signals

- Triangle wave. Specified by an amplitude and a frequency (or period).



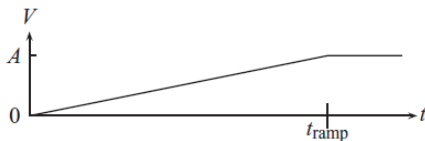
- Ramp. Specified by an amplitude and a ramp time.




# AC signals
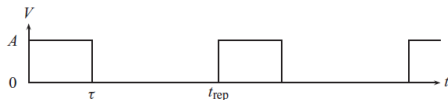
## Other signals

- Pulse train. Specified by an amplitude, a pulse width  $\tau$ , and a repetition time  $t_{rep}$ . The duty cycle of a pulse train is defined as  $\tau/t_{rep}$ .




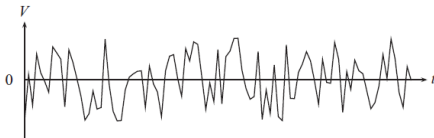- Noise. These are random signals of thermal origin or simply unwanted signals coupled into the circuit. Noise is usually described by its frequency content, but that is a more advanced topic.



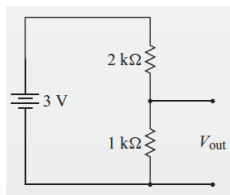
# Exercises

- The output of the voltage divider of Fig. 1.32 is to be measured with voltmeters with input resistances of  $100\Omega$ ,  $1K\Omega$ ,  $50K\Omega$ , and  $1M\Omega$ . What voltage will each indicate?



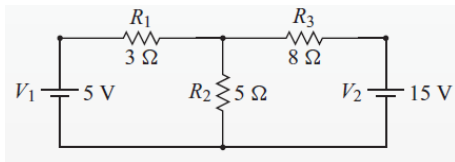- Compute the current through  $R_2$  and  $R_3$



Hint: use the superposition principle



- Basic Electronics for Scientists and Engineers, D. Eggleston, 2nd Ed  
Chap 1
- Kirchhoff's Law, Junction & Loop Rule, Ohm's Law - KCL & KVL  
Circuit Analysis