


# Introduction to Measurements Systems

## Real Opamps

### LA-CoNGA physics - 2024

by Dennis Cazar Ramírez

March 15, 2024

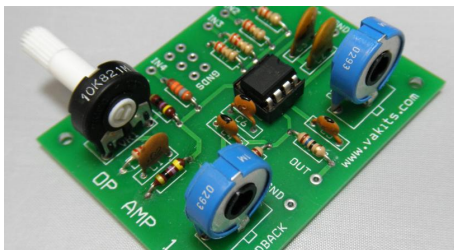

- How op-amps works?
- Open Loop Gain, Closed Loop Gain
- Noise Gain
- Gain Bandwidth
- Slew Rate


The following are some ways actual Op Amps differ from ideal performance:

- **Finite open loop gain.** It is impossible in an actual opamp for the open loop gain to be truly infinite.
- **Offset voltage.** The input stage of the op amp consists of a differential pair of transistors
- **Bias current.** The transistor inputs actually do draw some current.
- **Noise gain.** An opamp amplifies the signal and its noise.
- **Slew rate.** Capacitive effects in opamps set a finite speed of response

# Operational Amplifiers
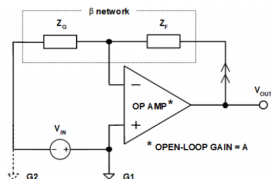
## Noise Gain $\beta$

- One of the most distinguishing features of op amps is their staggering magnitude of DC voltage gain. 100000 (100dB) for  $\mu A741$
- But in reality, op amps do have finite gain, and errors exist in practical circuits.



Feedback attenuation

$$\beta = \frac{Z_G}{Z_G + Z_F} = \frac{1}{G_{noise}}$$

# Operational Amplifiers

## Noise Gain


- Noise gain can now be simply defined as: The inverse of the net feedback attenuation from the amplifier output to the feedback input.
- In other words, the inverse of the  $\beta$  network transfer function.
- This can ultimately be extended to include frequency dependence.  
item Noise gain can be abbreviated as NG.

$$G_{CL} = \frac{1}{\beta} \left( \frac{1}{1 + \frac{1}{A_{OL}\beta}} \right)$$

# Operational Amplifiers
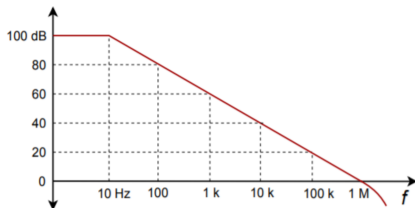
## Gain Bandwidth Product

- The open loop frequency response of a general-purpose op amp is shown in Figure.
- all devices will exhibit this same general shape and 20 dB per decade rolloff slope.




- **Gain Bandwidth** (GBW): The product of any break frequency and its corresponding gain is a constant. In other words, the gain decreases at the same rate at which the frequency increases.

# Non-linear applications
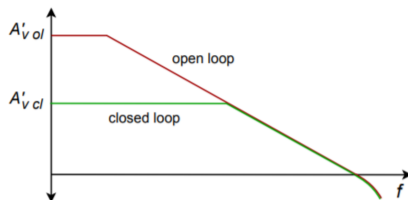
## GBW

- As you already know, operating an op amp with negative feedback lowers the midband gain.



- By knowing GBW and the gain, the associated break frequency can be quickly determined. For the inverting and non-inverting voltage amplifiers:

$$f_2 = \frac{GBW}{Gain}$$


# GBW calculations

## Example1

- Using a  $\mu A741$  op amp, what is the upper break frequency for a noninverting amplifier with a gain of 20 dB?
  - A  $\mu A741$  data sheet shows a typical GBW of 1MHz
  - Converting 20dB into ordinary form yields a gain of 10.

$$f_2 = \frac{GBW}{Gain} = \frac{1MHz}{10} = 10kHz$$

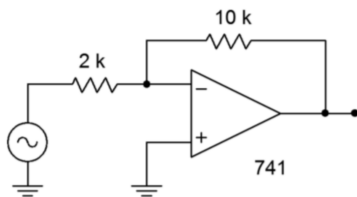- Sketch the frequency response of the circuit






# GBW calculations

## Example

- The resulting gain Bode plot

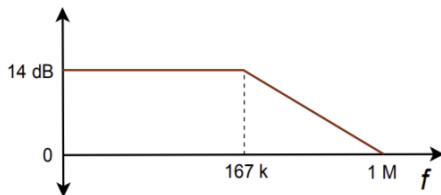

- where:


$$f_2 = 167\text{kHz}$$

- Let's simulate this circuit

# GBW calculations
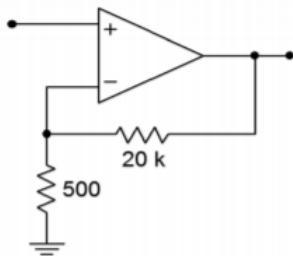
## Example

- Determine the minimum acceptable  $f_{unity}$  for the circuit if response should extend to at least  $50kHz$



- where:

$$f_{unity} = 2.05MHz$$

- Let's simulate this circuit

# Slew rate

## Definitions

- General-purpose op amps contain a compensation capacitor that is used to control the open loop frequency response.
- Due to this, the compensation capacitor can be charged no faster than a rate determined by the standard capacitor charge equation:

$$i = C \frac{dv}{dt}$$


$$\frac{dv}{dt} = \frac{i}{C}$$

- This quantity is called **Slew rate**, for a  $\mu A741$  op-amp  $SR = 0.5V/\mu s$


# Practical Considerations
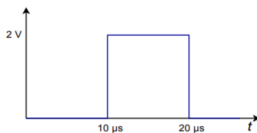
## The Effect of Slew Rate on Pulse Signals

- An ideal pulse waveform will shift from one level to the other instantaneously



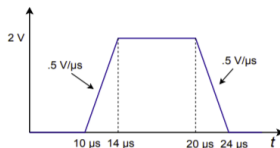- In reality, the rising and falling edges are limited by the slew rate.



- A  $\mu A741$  is used as part of a motor control system. If the highest reproducible frequency is 3 kHz and the maximum output level is 12 V peak, does slewing ever occur?
- An audio pre-amplifier needs to reproduce signals as high as 20 kHz. The maximum output swing is 10 V peak. What is the minimum acceptable slew rate for the op amp used?