

Latin-American alliance for capacity building in advanced physics

LA-CoNGA physics

Módulo de Instrumentación

Introducción a los Sistemas de Medida

Dennis Cazar Ramírez

Universidad San Francisco de Quito USFQ

18 - enero - 2021



Latin American alliance for
Capacity buildi**NG** in Advanced **physics**
LA-CoNGA physics



Cofinanciado por el
programa Erasmus+
de la Unión Europea



Universidad
Industrial de
Santander



Universidad San Francisco



YACHAY
TECH



UNIVERSIDAD
NACIONAL DE
INGENIERIA



UNMSM



frontier x
analytics



www.dbaaccess.com
DBACCESS



Introducción

Bienvenidos al Modulo de Instrumentación

- ▶ Toda la información del modulo se encuentra en la [LA-CoNGA GitmiLab](#)
- ▶ Ahora empezamos con el submódulo de Introducción a los sistemas de medida
- ▶ Este submódulo durará 4 semanas
- ▶ Tendremos 4 clases y 4 laboratorios

Temas de la clase

- ▶ Caracterización de circuitos AC
- ▶ Visualización de señales
- ▶ Análisis de señales
- ▶ Errores en medidas



AC circuits

- ▶ Currents and voltages that vary in time are called *AC* quantities
- ▶ AC circuits involves Resistances, Capacitors and Inductors
- ▶ Let's consider the response of an RC circuit to an AC signal V_{in} , KVL gives:

$$V_{in} = \frac{Q}{C} + IR \quad (1)$$

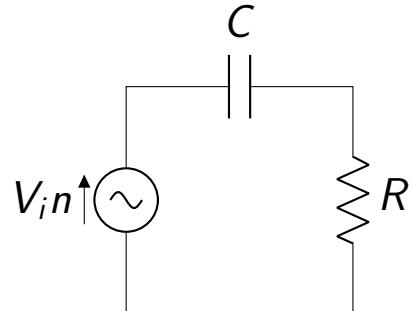


Figure 1: Simple RC circuit driven by a sinusoidal voltage..



Response to a step

- ▶ Let's assume that V_{in} is an step function ($V_{in}(t = 0) = 0$, $V_{in}(t = t_1) = V$)
- ▶ Taking the derivate of eq. (1)

$$0 = \frac{I}{C} + R \frac{dI}{dt} \quad (2)$$

- ▶ Solving for I we obtain:

$$I = I_0 \exp\left(-\frac{t}{RC}\right) \quad (3)$$

- ▶ Voltage drop in the capacitor is equal to:

$$V_c = V_{in} - IR \rightarrow V_c = V_{in} - I_0 R \exp\left(-\frac{t}{RC}\right) \quad (4)$$

- ▶ For future reference, we note that, since V_{in} and $I_0 R$ are constants, we can write a general solution for V_c as:


$$V_C = V_1 \exp\left(-\frac{t}{RC}\right) + V_2 \quad (5)$$

where V_1 and V_2 are constants.



Simulating the response

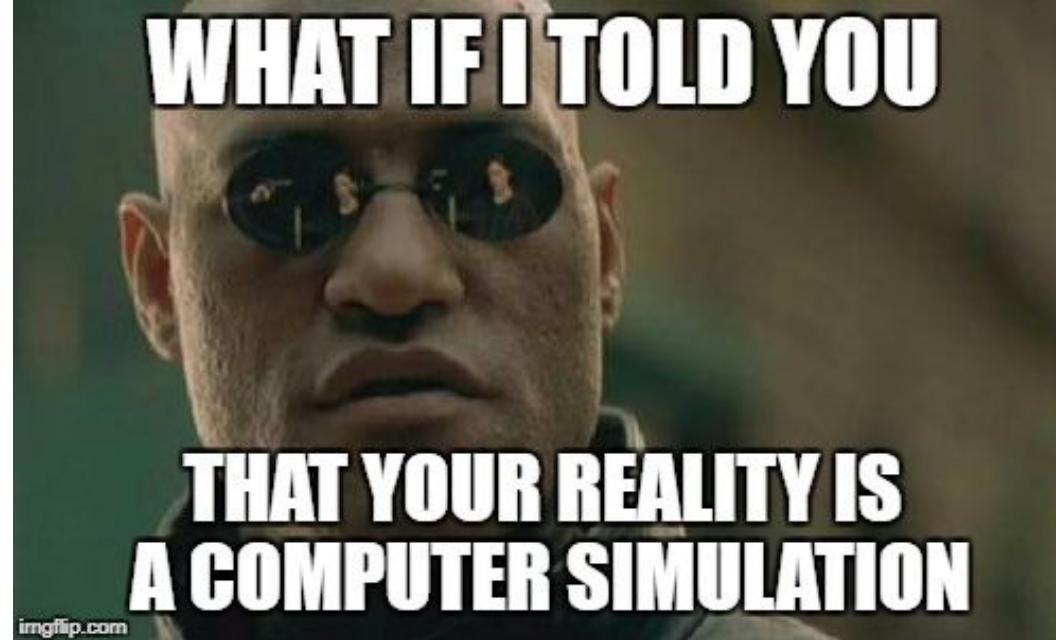- ▶ Let's simulate the response of this circuit using *LTS spice*





Response to a sine wave

and taking the time derivative of this and rearranging yields

$$R \frac{dI}{dt} + \frac{I}{C} = \frac{dV_{in}}{dt} \quad (6)$$

Note that, unlike the switching problem, the derivative of the input voltage is not zero. To solve eq.(2) we assume that:

- ▶ $V_{in} = V_p \sin \omega t$
- ▶ $I = I_p \sin(\omega t + \phi)$, where I_p and ϕ are constants to be determined

Replacing in eq(2) results in:

$$R\omega I_p \cos(\omega t + \phi) + \frac{I_p}{C} \sin(\omega t + \phi) = \omega V_p \cos \omega t \quad (7)$$

We now proceed to solve for I_p and ϕ .





Response to a sine wave

We obtain:

$$\left(\cos\phi + \frac{1}{\omega RC} \sin\phi - \frac{V_p}{I_p R} \right) \cos\omega t + \left(-\sin\phi + \frac{1}{\omega RC} \cos\phi \right) \sin\omega t = 0 \quad (8)$$

- At $t = 0$ equation (4) reduces to:

$$\cos\phi + \frac{1}{\omega RC} \sin\phi - \frac{V_p}{I_p R} = 0 \quad (9)$$

- Alternatively, if we choose t such that $\omega t = \frac{\pi}{2}$ we obtain:

$$-\sin\phi + \frac{1}{\omega RC} \cos\phi = 0 \quad (10)$$


- This last equation can now be solved for ϕ :

$$\frac{\sin\phi}{\cos\phi} = \frac{1}{\omega RC} \rightarrow \phi = \tan^{-1} \left(\frac{1}{\omega RC} \right) \quad (11)$$



Response to a sine wave

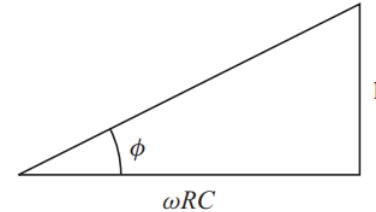- ▶ A right triangle satisfying Eq. (11) is shown in Fig. (2)



- ▶ It thus follows that

$$\sin\phi = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad \cos\phi = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \quad (12)$$

- ▶ Using these expressions in Eq. (9) and after some algebra

$$I_p = \frac{\omega C}{\sqrt{1 + (\omega RC)^2}} V_p \sin(\omega t + \phi) \quad (13)$$



Response to a sine wave

- ▶ Since we have already solved for the current, getting this output voltage is easy:

$$V_{out} = IR = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} V_p \sin(\omega t + \phi) \quad (14)$$

- ▶ we see that the output voltage has changed in two ways:
 - ▶ It has shifted in phase. Since $\omega RC > 0$ we have $0 < \phi < \pi/2$
 - ▶ The amplitude has changed. It is useful here to ignore the time variation and phase shift and simply compare the magnitude of the input signal $|V_{in}|$ with the magnitude of the output $|V_{out}|$:

$$\frac{|V_{out}|}{|V_{in}|} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \quad (15)$$

- ▶ Let's simulate the circuit response!