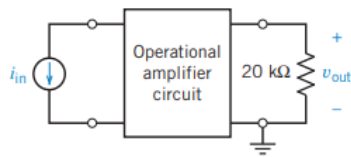


LA-CoNGA physics: Instrumentation Module


Introduction to Measurement Systems

February 12, 2021


1. Design the operational amplifier circuit in figure so that: $v_{out} = r \cdot i_{in}$, where $r = 20V/mA$



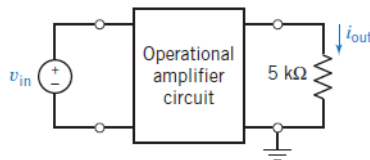
2. Design the operational amplifier circuit in figure so that: $i_{out} = g \cdot v_{in}$, where $g = 2mA/V$



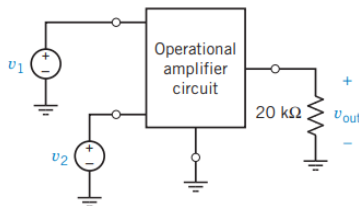
3. Design the operational amplifier circuit in figure so that: $v_{out} = 5 \cdot v_1 + 2 \cdot v_2$



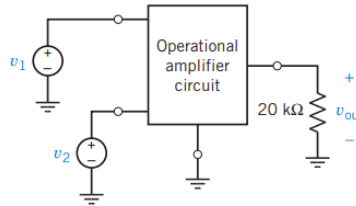
4. Design the operational amplifier circuit in figure so that: $v_{out} = 5 \cdot (v_1 - 2v_2)$



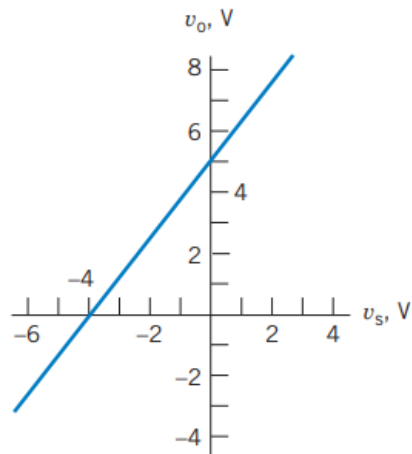
5. Design the circuit so that its input and output have the relationship specified by the graph shown, v_o is the output and v_s is the input



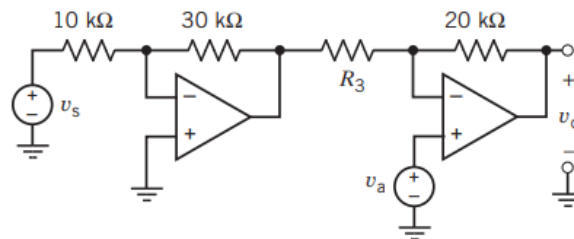
6. Specify values of R_3 and v_a that cause the output to be related to the input by the equation $v_o = 4 \cdot v_s + 7$



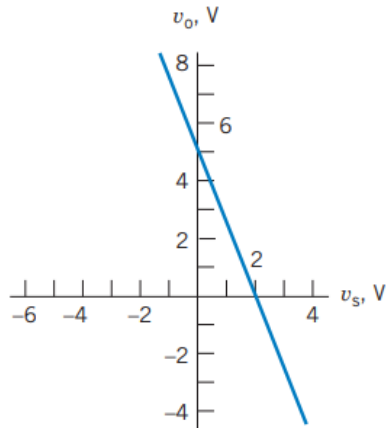7. Design the circuit so that its input and output have the relationship specified by the graph shown, v_o is the output and v_s is the input



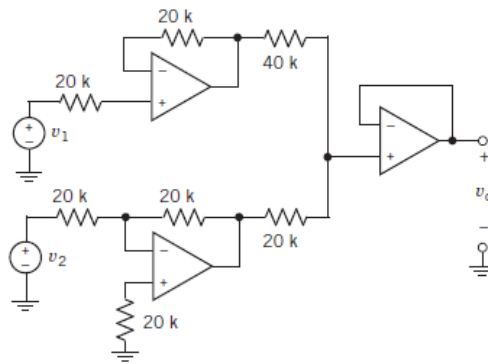8. Find out the relationship between v_o and v_1 and v_2 , the calculate the output for $v_1 = 80\mu V$ y $v_2 = 60\mu V$




9. Design a circuit having three inputs, v_1 , v_2 , v_3 , and two outputs, v_a , v_b , that are related by the equation

$$\begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} 12 & 3 & -2 \\ 8 & -6 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} + \begin{bmatrix} 2 \\ -4 \end{bmatrix}$$

Hint: A constant input is required. Assume that a 5-V source is available.

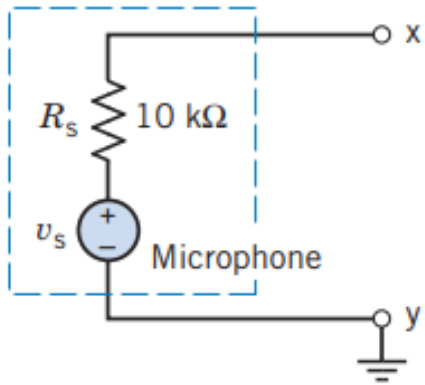10. A microphone has an unloaded voltage $v_s = 20mV$, as shown in figure. It is desired to provide an output voltage of 4 V. Design an inverting circuit and a non-inverting circuit and contrast the input resistance at terminals x-y seen by the microphone. Which configuration would you recommend to achieve good performance in spite of changes in the microphone resistance R_s ?



Hint: We plan to connect terminal a to terminal x and terminal b to terminal y or vice versa.